

# ECEN 5613: Embedded System Design

## Lab 1

Trevor Sribar

<https://canvas.colorado.edu/courses/130064/assignments/2624748>

# Table of Contents

<b>Table of Contents</b>	<b>2</b>
<b>Understanding Lab 1</b>	<b>3</b>
<b>Gaining Lab Access</b>	<b>4</b>
<b>Download Required Tools</b>	<b>4</b>
<b>Assembly Program</b>	<b>5</b>
Requirements:	5
Questions	5
Logic	5
Test Program	6
Above and Beyond	6
<b>Final Project</b>	<b>6</b>
Requirements	6
Timeline	7
Grading	7
Questions	7
Plans	7
References	8
<b>SPLD</b>	<b>8</b>
Microchip (Atmel) WinCUPL	9
WinSim	9
<b>Coding Atmel AT16V8C SPLD</b>	<b>11</b>
Assigning Pins	11
Generating of Outputs	11
Verification Vectors	12
Questions	12
Above and Beyond	12
<b>Checkoff</b>	<b>12</b>
<b>Obtaining Lab Kit</b>	<b>15</b>
<b>Basic Guide to Soldering</b>	<b>16</b>
<b>Handling Power Plastic Transistors</b>	<b>18</b>
<b>PCB Layout</b>	<b>18</b>
<b>Initial Hardware Design</b>	<b>19</b>
KiCad Basics	19
Implement core microcontroller design	20
Finalized Schematic	22
<b>Validating PCB</b>	<b>23</b>
<b>Layout of PCB</b>	<b>23</b>
<b>Labeling Your PCB</b>	<b>24</b>
<b>Inserting Wire Wrap Sockets</b>	<b>25</b>

<b>Power Circuit</b>	<b>25</b>
<b>Mounting the RS-232</b>	<b>27</b>
<b>Wire Standards</b>	<b>27</b>
<b>Wire Wrapping</b>	<b>28</b>
<b>Verification</b>	<b>28</b>
<b>Oscillator circuit</b>	<b>29</b>
<b>Pre-Programming</b>	<b>29</b>
<b>Programming</b>	<b>30</b>
<b>Validation of Circuit</b>	<b>31</b>
<b>Wiring the '373</b>	<b>32</b>
<b>Wiring the SPLD (F16V8B)</b>	<b>33</b>
<b>Loading Code to SPLD</b>	<b>34</b>
<b>Verifying Output</b>	<b>34</b>
<b>Oscilloscope:</b>	<b>36</b>
<b>Future steps</b>	<b>36</b>
<b>EFM8BB1/ARM</b>	<b>36</b>
<b>Questions and Check in</b>	<b>37</b>

# Overhead

## Understanding Lab 1

Lab 1 is split into 3 parts

### **Part 1 (due 1/16 2 PM):**

- Basic assembly language program
- Understand of said program
- Practice using testing practices (setting of accumulator and registers)
- Practice making well-commented code
- Gain a strong understanding for the final project for this class
- Learn how to use Microchip (Atmel) WinCUPL
- Learn how to use WinSim
- Review Tutorials for the two above tools
- Review the example code for the two above tools
- Use WinCUPL to make basic code for the Atmel AT16V8C SPLD

### **Part 2 (due 1/23 2 PM):**

- Buy a kit from a TA
- Verify kit has all parts & Acquire items for the semester
- Familiarize self with lab equipment locations
- Gain an understanding of soldering
- Learn how to treat electronics
- Gain an understanding of the schematics for our PCB
- Draw a schematic of your PCB
- Design the power, oscillator, and power on circuits

### **Part 3 (due 1/30 2 PM):**

- Ensure PCB doesn't have manufacturing defects
- Plan future layout
- Label the PCB
- Solder wire wrap sockets to PCB
- Solder power jack to PCB
- Wire power jack and switch to PCB
- Solder RS-232 to PCB
- Create standard for color for wire wrapping
- Learn and use wire wrapping
- Verify integrity of solders and wraps
- Verify Power
- Create basic wiring for 8051
- Program 8051
- Verify 8051 integrity
- Verify VCC voltage & ripple
- Wire the '373 latch

- Test digital logic for AT16V8C
- Learn about O-Scopes
- Create steps to complete base board
- Learn about ARM/EFM8BB1 architecture

## Gaining Lab Access

I already have lab access from being in the course as seen in Fig 0.1.



**Fig 0.1: Access to Lab**

## Download Required Tools

The tools we will use are:

Keil uVision debugger for C51 or the SilabsEFM8BB1 dev board with Simplicity Studio  
Canvas has the file location and demo videos of using them from the TAs

# Part 1

## Assembly Program

### Requirements:

Implement the equation  $X^4 / Y = Z$

- Do not use MUL or DIV
- Use shift(s) to implement  $X^4$
- Program starts at 0x000h
- ENDLOOP exists and program always ends in it (infinite loop)

X, Y, and output Z are uint8s

X: Starts in the accumulator

- throws an error 0x02 in Error location if overflows after \*2 and ENDS

Y: Starts in B register

- throws an error 0x01 in Error location if is 0 and ENDS

End conditions:

IRAM location 0x20 contains the value of (X)

IRAM location 0x21 contains the value of ( $X^4$ )

IRAM location 0x22 contains the value of (Y)

IRAM location 0x23 contains Z, the 8-bit quotient (in hexadecimal)

IRAM location 0x24 contains the 8-bit remainder (in hexadecimal)

IRAM location 0x30 contains the error code.

(IRAM means Internal Data Memory)

### Questions

Does 0x20, 21, and 22 have how big of a size? A byte probably

### Logic

Shift Left 2 in order to multiply X

See if there is an easy way to check 2 leftmost bits for being 1

- Shift left and check if non-zero
- And both bits and OR them
- Subtract after shift and see if is a smaller number?

Check if Y is zero

Then go through operations

Division

- Initialize 0x23 to 0

- Check if  $X-Y < 0$  (we checked if  $X-Y$  causes carry to be set)
- If yes, set 0x24 to  $X \& END$  (make sure to set 0x00 to error location)
- If no, let new  $X = X-Y$  and add 1 to 0x23, then repeat

Strange Parts of implementation

- We check for overflow in subtraction in order to find when to end the loop
  - This causes us to have no value to save to the remainder register
  - We have to add back  $Y$  to this overflowed  $W$  in order to get back the remainder

## Test Program

setting the accumulator and B register to various initial values

Use combined code and data space in the 8051 (/overlay option if using Emily52)

### **How to set values in data space**

Load into debugger => bits on left, double click to change

### **How I set values in code**

Added a “Preconditions” Section, which can be seen in lab1Part1\_1WithPre

## Above and Beyond

Create the DIV and MULT version in a different location after our original run, then subtract the values and check if both are 0. If not, throw a new error.

## Final Project

### Requirements

8-9 minute demo (including a power point)

Establish goals

- Individual or Groups of 2
- Electronics & Firmware > Software, Mechanical, Packaging
- New hardware
- New firmware
- ~5 min PDR
  - Overview
  - Milestones
  - Deliverables
- No risk to students
- Each team member present for demos
  - This includes a presentation
  - Includes a detailed block diagram
  - Talk about design/implementation
  - Talk about struggles

- Demon night class might (will) go late & start early
- A video of the working project
- All files are .pptx .mp4 or .pdf
- Final lab doc
- Honor code signed
- Files
  - All project files (code in source + pdf, header files, make files, ect., & other docs such as unique data sheets, and notes)
  - Organized fileset
- One copy of everything into canvas
- Report
  - Keep big stuff at end
  - Page numbers, cover page, ect.
  - Word editor
  - Don't include details about labs 1-4
  - Title (descriptive) names, ect.
  - Division of labor
- Don't copy onlines stuff
  - Or make sure it's legal & well documented before hand
- Code headers must have name, revision, date, important code

## Timeline

Ideas by Late Feb

PDR Submission Sunday, March 8th

PDR Presentation Tuesday, March 10th

Final Demo by April 24th

Documentation by April 29th

## Grading

38% of your grade

Must be complicated (no arduino)

Idk bro

## Questions

Can I write my report in docs?

Where is the rubric?

## Plans

Printer

Contactless doom (PS2 connectors)

## Jane-street style algorithmic microtrades

- Trades are FPGAs
- Fall PLES

## References

Final project posted on Canvas: [https://canvas.colorado.edu/...](https://canvas.colorado.edu/)

Mp4s under canvas previous projects: (on canvas aswell)

## SPLD

SPLD stands for

Download Atmel WinCUPL tools:


<https://canvas.colorado.edu/courses/130064/pages/ecen-5613-reference-files-and-links>

The following documents will be useful for HW #2 and Lab #1:

- National Semiconductor (now TI) LM7800C/LM140/LM340 Voltage Regulator Data Sheet: [PDF](#) (~513KB)
- Motorola MC7800 Voltage Regulator Data Sheet: [PDF](#) (~279KB)
- Intel AP-125 Designing Microcontroller Systems for Electrically Noisy Environments: [PDF](#) (~454KB)
- Intel AP-711 EMI Design Techniques for Microcontrollers in Automotive Applications: [PDF](#) (~409KB)
- TI SCBA007A The Bypass Capacitor in High-Speed Environments: [PDF](#) (~68KB)
- Intel AP-155 Oscillators for Microcontrollers: [PDF](#) (~979KB)
- Microchip AN686 Understanding and Using Supervisory Circuits: [PDF](#) (~93KB)
- Microchip MCP-101 Microcontroller Supervisory Circuit Data Sheet: [PDF](#) (~243KB)
- Maxim MAX691 Microprocessor Supervisory Circuit Data Sheet: [PDF](#) (~627KB)
- Maxim MAX805L Microprocessor Supervisory Circuit Data Sheet: [PDF](#) (~99KB)
- Tektronix Primer XYZs of Oscilloscopes: [PDF](#) (~622KB)
- Tektronix Primer ABCs of Probes: [PDF](#) (~945KB)
- Microchip (Atmel) ATF16V8C SPLD Data Sheet and Software:
  - ATF16V8C Datasheet: [PDF](#) (~512KB) . [Microchip \(Atmel\) ATF16V8C Link](#)
  - Microchip/Atmel [WinCUPL Link](#) . [WinCUPL Installation Executable](#) (~21MB) . [WinCUPL Installation Executable Zip file](#) (~21MB)
  - [WinCUPL User's Guide](#): [PDF](#) (~350KB)
  - [WinCUPL Tutorial and Supporting Docs](#): [ZIP](#) (~134KB)
  - Running [WinCUPL](#) in an Ubuntu Virtual Machine with Wine: [PDF](#) (~70KB)
  - Introduction to Atmel ATF16V8C and [WinCUPL](#) (lecture notes): [PDF](#) (~287KB)
- Device Programmer (Phyton ChipProg-48, Needham's EMP-20/EMP-100)
  - ATF16V8C SPLD Programming Guide for Phyton ChipProg-48: [PDF](#) (~343KB)
  - [Archive] ATF16V8C SPLD Programming Guide for NEI EMP-100: [PDF](#) (~136KB)
  - [Archive] EMP-20 Device Programmer Presentation Handouts (1-30-2005): [PDF](#) (~177KB)

Fig 1.3.1: Where WinCUPL installation is on Canvas

## Microchip (Atmel) WinCUPL

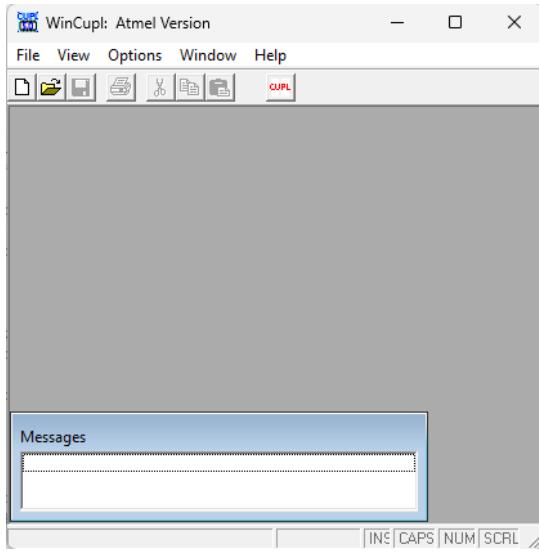

**Fig 1.3.2: Initial view of WinCUPL**

## WinSim

File Structure (from the class handout found on canvas)

```
Name          Gates08;  
Partno       ESD001;  
Revision     01;  
Date         1/22/2008;  
Designer    I.M. Good;  
Company      University of Colorado;  
Location     None;  
Assembly    None;  
Device       g16v8a;  
  
/******************************************/  
/*  
/*      General File Comments  
/*  
/******************************************/  
  
/*  
* Order: define order, polarity, and output spacing of stimulus and response values  
*/  
  
/*  
* Vectors: define stimulus and response values, with header  
* and intermediate messages for the simulator listing.  
*  
* Note: Don't Care state (X) on inputs is reflected in outputs where appropriate.  
*/
```

**Tip:** Header information for WinCUPL source file (.PLD) and WinSim input file (.SI) must match.

**Fig 1.3.2: Header layout of file**

Running/Compiling:

1. Go to Run => Device Specific Compile (check warnings/errors)
2. Double Click .si file

### 3. Simulator => Run Simulation

#### Creating Inputs/outputs

- Should be: pin (#) = (internal designation)
  - Can be [(char)#..0]

#### Operators (manual)

- & = and
- ! = not
- # = or
- \$ = XOR
- \*\* = Exponential
- \* = Multiplication
- / = Division
- % = Modulus
- + = Addition
- - = Subtraction

#### Creating Numbers (manual)

- 'b'0 Small Binary
- 'B'0000 Big Binary
- 'D'55 Decimal
- 'h'1F hex
- 'H'AX11 Hex (X characters are for don't cares/range of vals)

#### Fields (manual)

- Basically arrays
- FIELD ADDRESS = [AX..A0];
- FIELD DATA = [DX..D0];
- FIELD Mode = [Up, Down, Hold];

Logs & Flip-Flops are on pages 15&16 of the manual, hopefully you won't need them

#### Test Vectors

```
ORDER: clock, input1, input2 , !output ;
VECTORS:
P X X 1 /* reset flip-flop */
           /* !Q goes to 1 */
           /* Q goes to 0 */
0 X X H /* output is HI due to */
           /* inverting buffer */
```

**Fig 1.3.3: Help menu documentation of Test Vectors**

This does not work. I cannot find the file that this would be in. Instead, Do these steps

1. Have working code
2. Open the simulator by hitting the window with lines at the top

3. File->new
4. Select the project you have working code for using the box on the right
5. Add all signals (input/outputs) by clicking on the left/"addsignal" button on the top
6. Add the vectors you want by hitting the "add vector" button on the top
7. Manually click all signals into states that you want to see the output of

General Notes (From tutorial and class handout)

- If you get rid of any of the wanted "windows", just go to view
- Options
  - Compiler => CUPL compiler
    - Fuse Plot
    - Equations
  - Device => opens device select
    - Device (select ATF22V10B)
    - Mnemonic g22v10
  - Simulator => Sets simulation options
  - WinCUPL => Sets WinCUPL environment
- Help can be found at any time on the top
- Changing headers must be changed in both locations (or you will get warnings)
- Negative polarity on output pins doesn't work (but will compile)
- If you want to compare values across FIELDS (arrays), you must add bits as don't cares
  - CSROM = !(ADDR:0xxx # ADDR:1xxx # ADDR:2xxx # ADDR:3xxx # ADDR:4xxx  
# ADDR:5xxx);
  - CSROM = !(ADDR:[0xxx..5xxx]); /\* CSROM low for addresses 0000h-5FFFh \*/

## Coding Atmel AT16V8C SPLD

### Assigning Pins

Requirements: Assign A15, A14, A13, A12, /RD, and /PSEN

Finding Pins: the datasheet for the AT16V8C doesn't have specified A15-12, so I will just use I/O pins, which 15-12 are conveniently open, so I will use those.

16 & 17 are also not used, so I will use those for /RD and /PSEN respectively

That did not work, as pin 16 got angry at me and A14 was an invalid input, trying with 8-5 as the "A"s and 2 & 3 as the /RD and /PSEN.

### Generating of Outputs

Requirements: READ\_n = RD\_n & PSEN\_n, and CSPERIPH\_n = !(A15 & A14 & A13 & A12)

I don't know if we will need output pins, but I will use the last two, 18 and 19, on this side of the processor.

- \_n means active low

## Verification Vectors

Requirements:

- >= six test vectors to show correct logic functionality (well-chosen subset of input conditions)
- READ\_n output of the SPLD should toggle on either /RD or /PSEN toggles
- CSPERIPH\_n should be
  - high most of the time
  - low only for addresses in the range of F000h-FFFFh

## Questions

Why did pin 14 not want to be an input if it is labeled as IO on the technical documentation?  
Why just that pin and not the others?

## Above and Beyond

Created 16 vectors, one for each of the states

## Checkoff

1. Show the TA your code and full listing (e.g. .LST) file
2. (Final project) Show understanding of and discuss your questions with the TA during the Part 1+2 signoff.
3. Show the TA your commented .PLD source file and .SI simulator input file
4. Explain how these files are structured

Upload Lab 1 Part 1 files in a zip file

- named: "lastname\_lab\_1\_signoff\_sw.zip"
- three folders
  - "Spld"
  - "8051"
  - "other\_files"
- The WinCUPL code file must be placed in the "spld" folder
- The assembly .lst file must be placed in the "8051" folder
- Your answers to the following questions (in a PDF file) must be placed in the "other\_files" folder.

**How many bytes of code space does your program require?**

Code Size? 51 bytes.

I found this by removing the preconditions (with them it would be 56 bytes) and building the project. Then I checked the build window for the byte size as seen in Fig 1.5.1:

```

Build Output
Build started: Project: Lab1Pat1.1
Build target 'Target_1'
assembling lab1Pat1_1.asm...
linking...
Program Size: data=8.0 xdata=0 code=51
".\Objects\Lab1Pat1.1" - 0 Error(s), 0 Warning(s).
Build Time Elapsed: 00:00:00


```

**Fig 1.5.1: Build file output (without preconditions)**

**How long did your program take to execute for X=0x33 and Y=0x07? Assume an 11.0592 MHz clock and include the instructions executed from the beginning until you reach the ENDLOOP label.**

Execution Time? 17.6323784722 us

Calculations can be seen in Fig 1.5.2

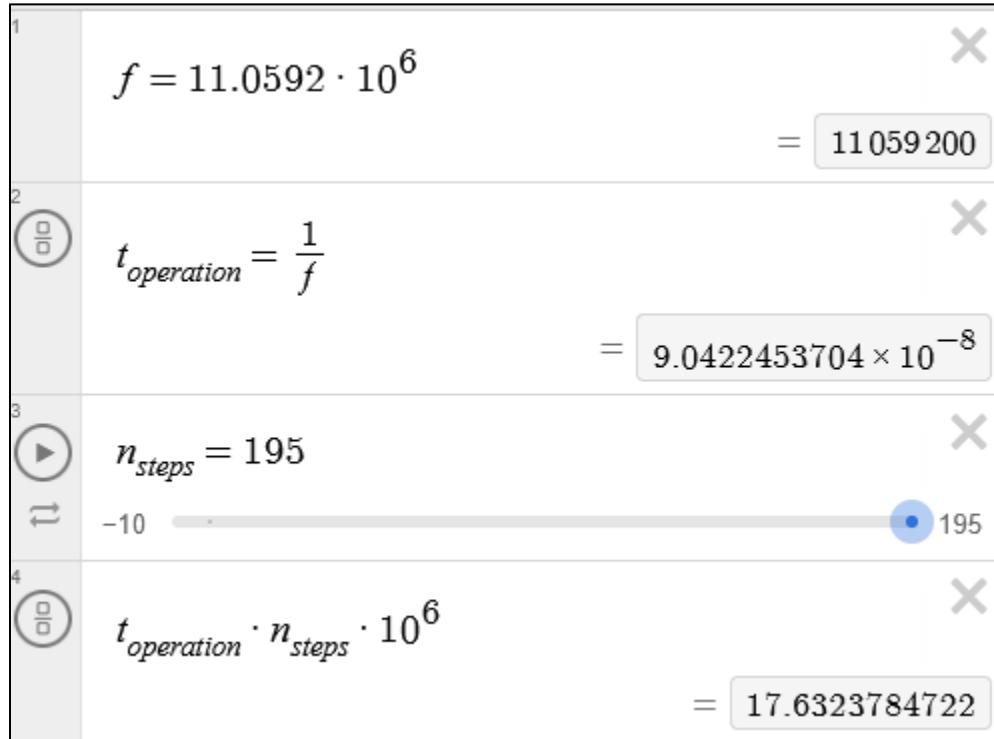

**Fig 1.5.2: Detailed Calculation**

The way  $n_{steps}$  was found was by running the code with a breakpoint at ENDLOOP and checking the machine states after reaching said loop, which was 195, as seen in Fig 1.5.3

Register	Value
r0	0x00
r1	0x00
r2	0x00
r3	0x00
r4	0x00
r5	0x00
r6	0x00
r7	0x00
a	0x01
b	0x07
sp	0x00
sp_max	0x07
dptr	0x0000
PC \$	C:0x0031
states	195
sec	0.00005850
+ psw	0xc1

Fig 1.5.3: Register display after running code to ENDLOOP

# Part 2

## Obtaining Lab Kit

I have paid over VENMO as seen in Fig 2.1.

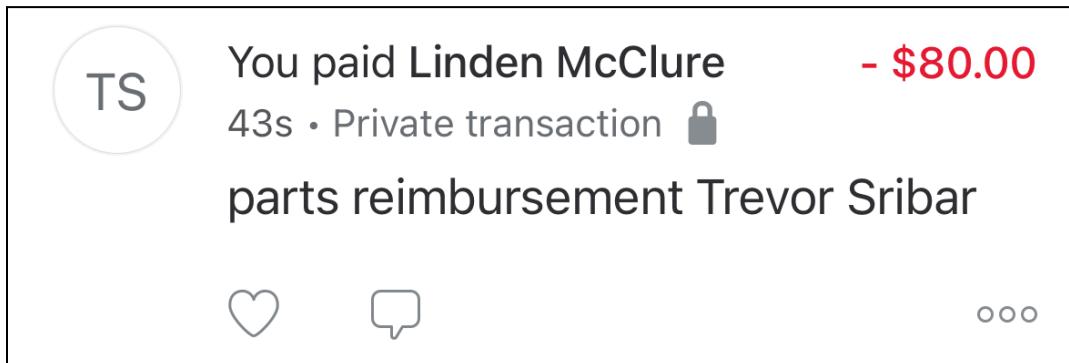


Fig 2.1: Evidence for paying for parts kit

### BIG BAG

Printed Circuit Board 1:	1
16x4 LCD with HD44780 Compatible Controller:	1

### SMALL BAG 1

40-Pin Wire Wrap DIP Socket (0.6" wide):	1
28-Pin Wire Wrap DIP Socket (0.6" wide):	1
20-Pin Wire Wrap DIP Socket (0.3" wide) x4:	4
16-Pin Wire Wrap DIP Socket (0.3" wide) x3:	3
14-Pin Wire Wrap DIP Socket (0.3" wide) x2:	2
8-Pin Wire Wrap DIP Socket (0.3" wide):	1
Pin Strip Socket, Single Row, 14 Contacts:	1
Pin Strip Header, Single Row, 36 Contacts x2:	2
Aluminum Standoff, Female/Female, 6-32 x4:	4
Aluminum Standoff, Male/Female, 6-32 x4:	4
DE-9 Serial Connector:	1
TO-220 Heat Sink:	1
2.1mm Male Power Connector:	1
Toggle Switch, SPST or SPDT:	1

### SMALL BAG 2

T44 Wire Wrap Pins x20:	25 (forks)
Pushbutton Switch, Momentary x4:	4

Jumper/Shorting Block x5:	5 (Little blue squares)
7805T +5V Regulator, TO-220 Package:	1 (7805T)
11.0592 MHz Crystal:	1
27 pF Capacitor x3:	3
47 uF Electrolytic Capacitor x2:	2
10 uF Electrolytic Capacitor x2:	2
0.1 uF Monolithic Ceramic Capacitor (>=10V) x10:	10 104s
1.0 uF Monolithic Ceramic Capacitor (>=16V) x5:	5
4.7 uF Monolithic Ceramic Capacitor (>=10V) x2:	2
Diode, 1N4003 (1 Amp) x5:	5 (Black diodes)
Diode, 1N914 or 1N4148:	1 (Red diode)
10K 1/4W Resistor:	1 (Brown Black O G)
4.7K (or 2.7K) Pull-up Resistors, 10-pin SIP x2:	2
330 Ohm 1/4W Resistor x5:	5 (O O B G)
5.1K Ohm 1/4W Resistor x2:	2 (G B O G)
Potentiometer:	1
LED, Red x2:	2
LED, Green x2:	2
2N2222 NPN Transistor, TO-92 x2:	2 (PN 2222)
2N2907 PNP Transistor, TO-92 x2:	2 (IPS, 2907A)

### Narrow Tube

74LS373, Transparent Latch, Tri-state, DIP-20:	1(GD74...)
74LS374, Octal D Flip-Flop, Tri-state, DIP-20:	1
MAX 232, RS-232 Line Driver/Receiver, DIP-16:	1
24C16 Serial EEPROM, DIP-8:	1
PCF8574 I2C I/O Expander, DIP-16:	1
SPI DAC (e.g. Microchip MCP4802), DIP-8:	1
SPLD (e.g. Microchip ATF16V8B/C), DIP-20:	1
8051, (Microchip/Atmel) AT89C51RC2, DIP-40	1 (isolated)

## Basic Guide to Soldering

Tools:

- Soldering Iron
- Sponge to wipe iron off on
- Flux
- Exhaust Fan (on)
- Solder
- Mat
- Tip Tinner
- Solder Sucker

Pre-Conditions



**Fig 2.2.1: Iron with condensate ([link](#))**

If the iron looks like the one above, take it to a file

When starting, melt a bit of solder onto the tip and then rotate it in the sponge (or use tip tinner)

#### Instructions

- Wet sponge (if using a wet sponge, distilled water)
- Turn soldering iron on to temp you want
  - Lead = 600 - 650°F
  - Non-lead = 650 - 700°F
- Heat what you want to add solder to
- Apply solder to side of the tip of the iron while right next to component
- Guide the solder onto where you want it

#### Why use flux?

[Guide to Soldering](#): “Without flux the solder would oxidize rapidly, not flow efficiently, and result in poorer joints.”

It is the stuff that smokes when you push solder onto the iron (apply solder fast!)

#### Why is flux used?

Flux is used as it pulls the layer of oxidation off the surface of metals, allowing them to properly merge together. It also aids “wetting”, the ability for metal to adhere to solder. It also dissipates heat evenly across parts.

#### What type of flux should be used with electronic circuits?

Rosin, No-Clean, or Aqueous as followed by the IPC J standard.

#### Will flux remove grease from a connection point?

No, clean the board beforehand

### **What is a cold solder joint, and how is it created?**

A solder that appears to bridge a connection but is unreliable/doesn't work at all.

"Characteristics of cold solder joints include a rough surface area, rigidity, and a generally uneven appearance" [Understanding Cold Solder Joints](#). They often form when the PCB or part is not heated enough.

## **Handling Power Plastic Transistors**

When bending/cutting

- Hold where the pins will break off/bend (not the resin)
- Don't bend pins more than once
- Don't bend pins more than 90
- Don't bend pins "out" from the sides

PCB mounting

- Leave space between PCB & Circuit (spacers help)

Soldering


- Try to minimize high-temp exposure
- Remove excess flux, don't use trichloroethylene based products

Mounting Heat Sink


- Some have a screw you can use
- Others just use a spring clamp (paper binding)
- Don't mount them too tight (breaking plastic/copper)
- Silicone grease can help with conductivity (not too much)

## **PCB Layout**

All of these are from the [reference file](#)

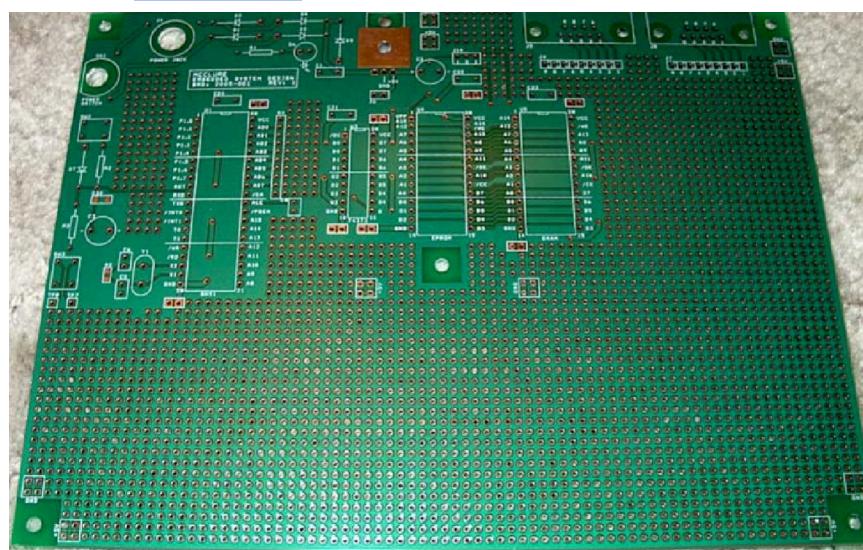

**Fig 2.4.1: TOP side of PCB, notice that Decoupling capacitors on the top left**

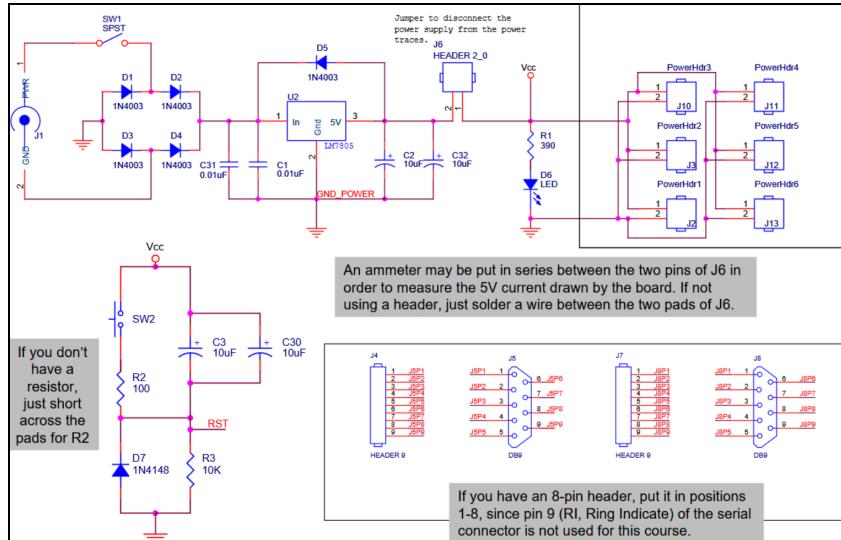


**Fig 2.4.2: Basic Circuits used on PCB**

Size is 6" by 8"

## Initial Hardware Design

Software Choice: KiCad

### KiCad Basics

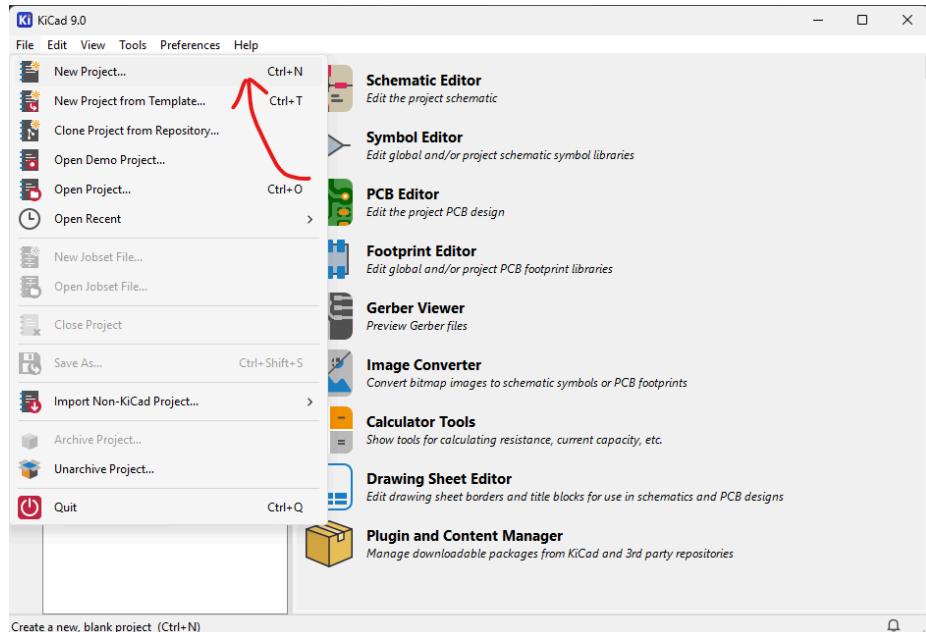

**Fig 2.5.1: Making a new project**

1. Find the directory you want the project in
2. Write the project name
3. Go into the Schematic editor for the project

#### Adding Symbols

1. Place => Symbols (or A)
2. Search up your symbol

#### Renaming Symbols

1. Right click => Properties
2. Click to rename "Value"

#### Labeling Areas

1. Place => Draw Text Boxes
2. Click once, then drag to size you want, then click again
3. Name what you want it and click "OK"


## Implement core microcontroller design

#### Basic Circuit Elements


- 8051
  - Power on circuit
  - Runtime circuit
- 11.0592MHz Oscillator
- 7805 (or 340T5) +5V regulator
- Hardware
  - PCB
  - Standoffs
  - Power Connector
  - 9-pin RS-232 Connector
  - Ect
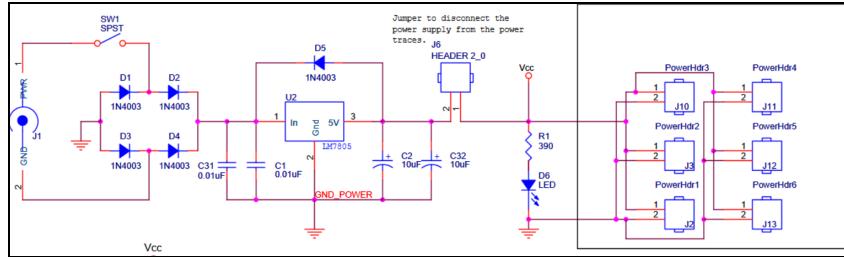
#### Design:

- Power circuit
  - 2.1mm power jack (3 pin barrel)
  - power switch (DPDT)
  - Diode bridge (to allow two different wall adapter connector polarities – center positive or center negative) (1N4003)
  - 7805 voltage regulator
  - power-on LED




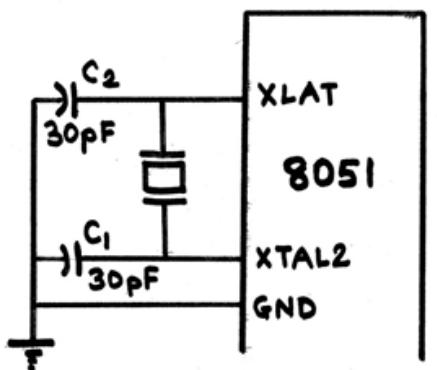- C31 and C32 are not through-hole capacitors, so I did not add them
  - Changed resistance to 330 as that is what I have in my kit
  - Oscillator circuit
    - Crystal
    - 27pF capacitor



([link](#))

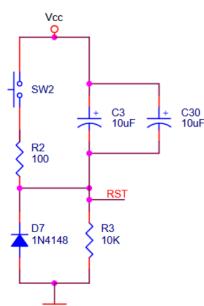- Power On Rest Circuit
    - RC
    - Pushbutton



- Replaced R2 with a 330 ohm and R3 with 5.1k ohm, as this is what our kit has
  - C30 is not a through-hole capacitor, so I did not add it

## Finalized Schematic

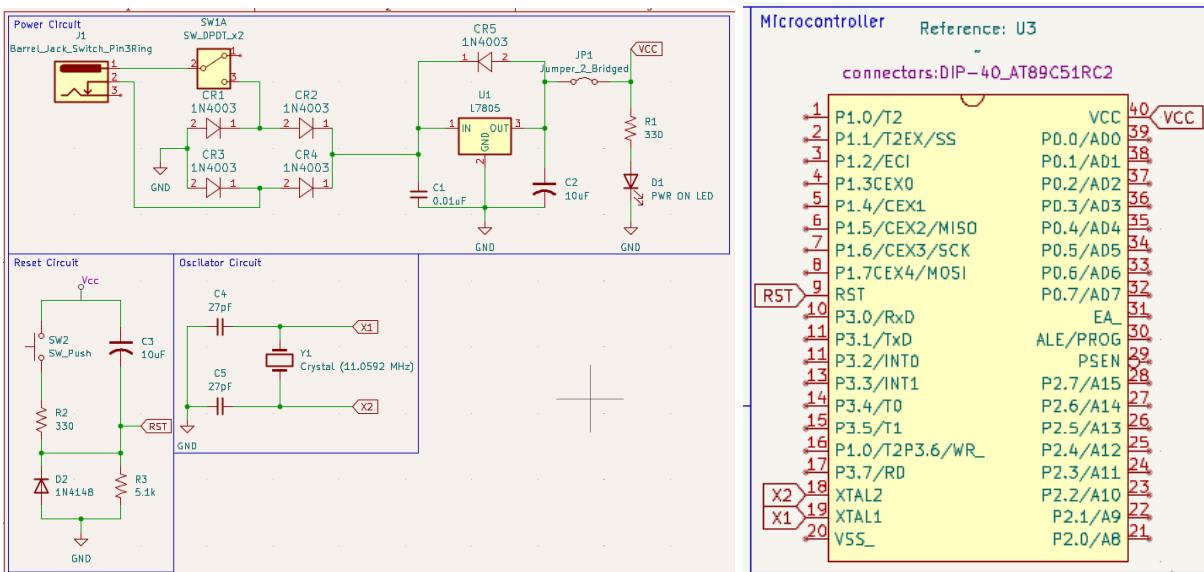


Fig 2.5.2: Schematic for part 2

# Part 3

## Validating PCB

I probed continuity to all GND lines and continuity of all 5 V lines, which all had continuity. Then I probed a ground to 5 V, meaning none of the ground lines have continuity with any of the 5 V lines.

## Layout of PCB


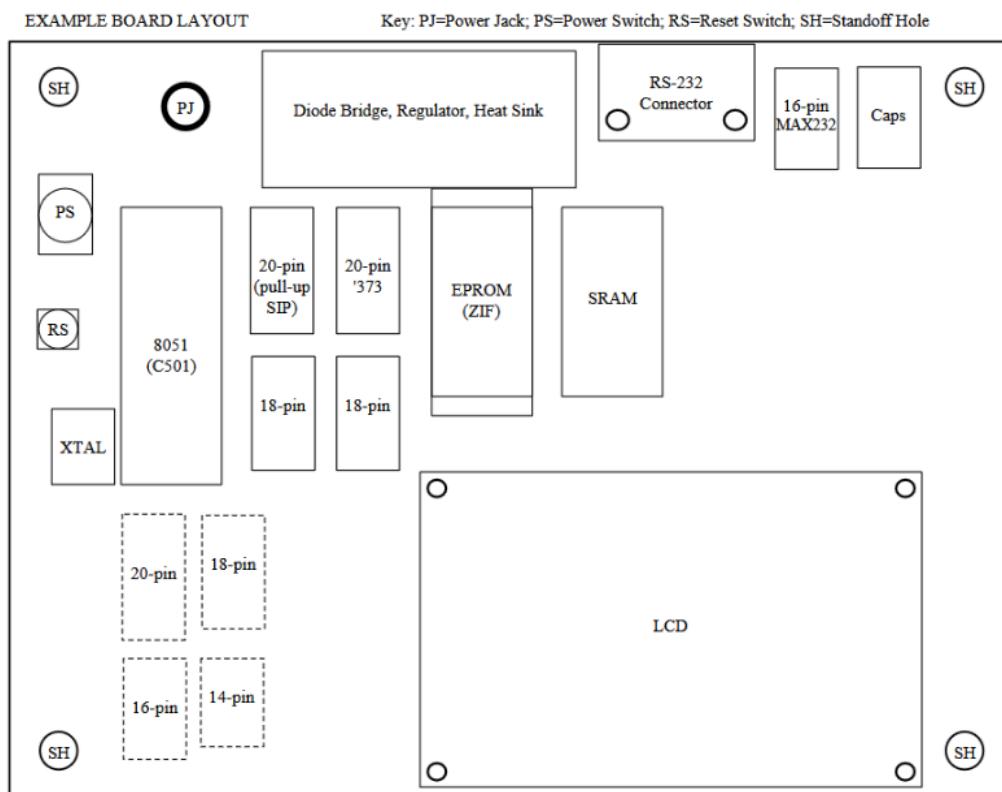


Fig 3.2.1: Example layout of PCB from Canvas

### Notes


- leave a keep-out area (perhaps 0.5" to 0.8" wide) around the edge (cracking)
- Serial port connector and Power Supply Connector on the same edge of board for ez turing over
- Reset button and power supply SW near edge of board (EZ upside down reach)
- Buttons/Switches/Jacks EZ for fingers to reach (less components around them)
- Micro to pull-up resistors, 74LS08, 74LS373, SRAM, **oscillator** close
- 10-100nF for bypass caps for each chip **small loop**
- Drill early/not at all

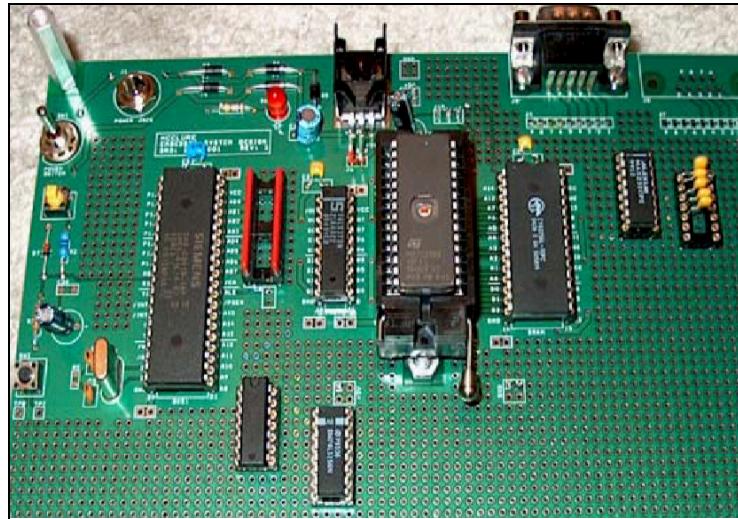

**Fig 3.2.2: Example Board Setup (partial schematic canvas)**


Due to not knowing all the components and what each will need, it is hard to make a final schematic, so I will try to put bypass caps at the heads of all the ICs as a convention, and follow this diagram when I am unsure of what to do next.

## Labeling Your PCB

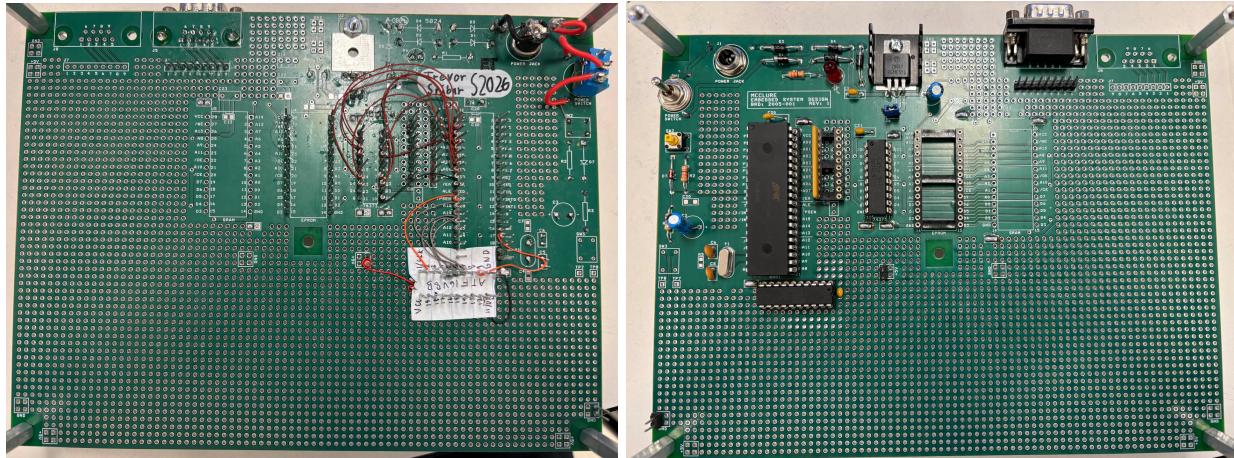

**Fig 3.2.3: Images of labeled PCB**

# Inserting Wire Wrap Sockets

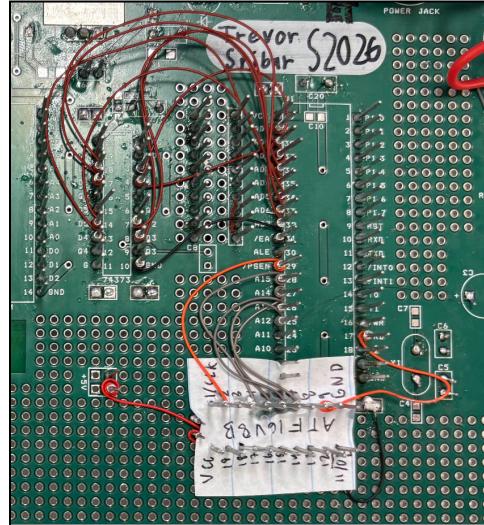

**Fig: 3.2.4: image of circuit with wire wrapping**

I am unsure of what the other parts are that I may need, I have added the obvious/non unlabeled wire wrap sockets, but have left the others off for now.

## Power Circuit

Screw in:


- Power jack header
- Switch

Solder in:

- 8705T
- Diodes x5
- 330 ohm resistor R1
- RED power LED
- 100nF capacitor C1 (changed from 10nF as it wasn't in parts kit)
- 10uF capacitor C2


Solder for the switch:

- 330 ohm resistor R2
- Switch SW2
- Power Switch SW1 and attaching wires
- 1N4148 Diode D7
- 5.1k ohm resistor R3
- 10uF capacitor C3

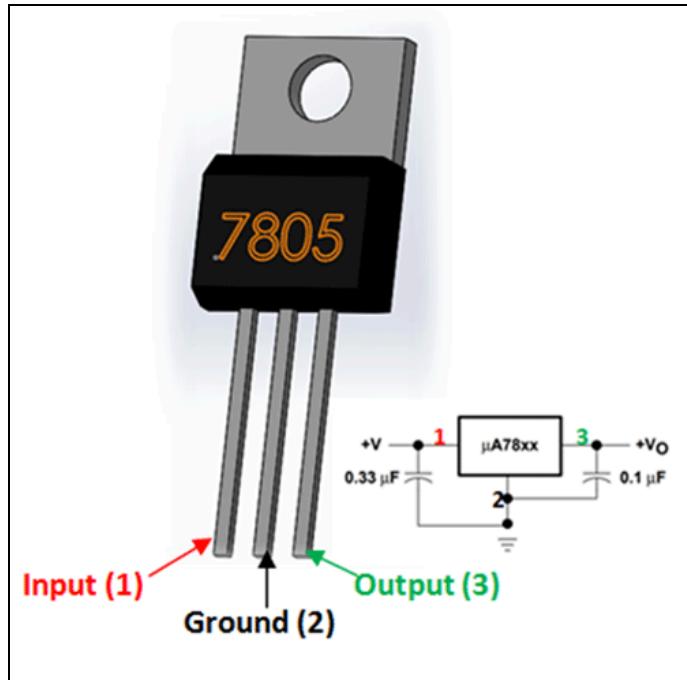

**Fig 3.3.1: 7805 pinouts labeled ([link](#))**

We can also attach the heat-sinc. I made sure to not hold the housing when bending the pins

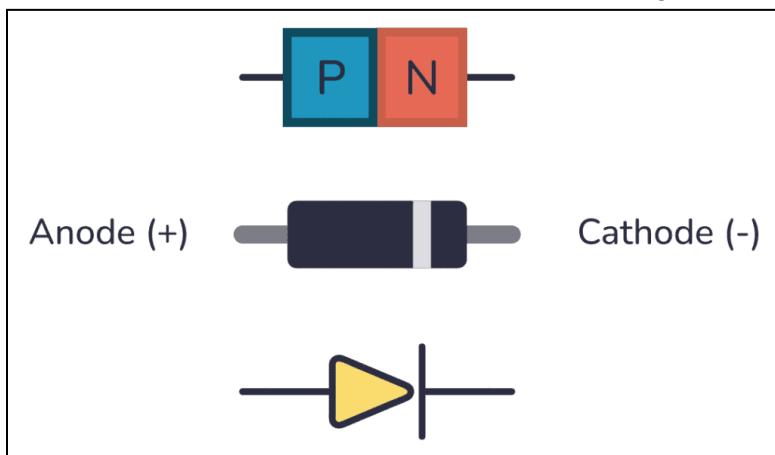

**Fig 3.3.2: Diode Anode and Cathode Labeled ([link](#))**

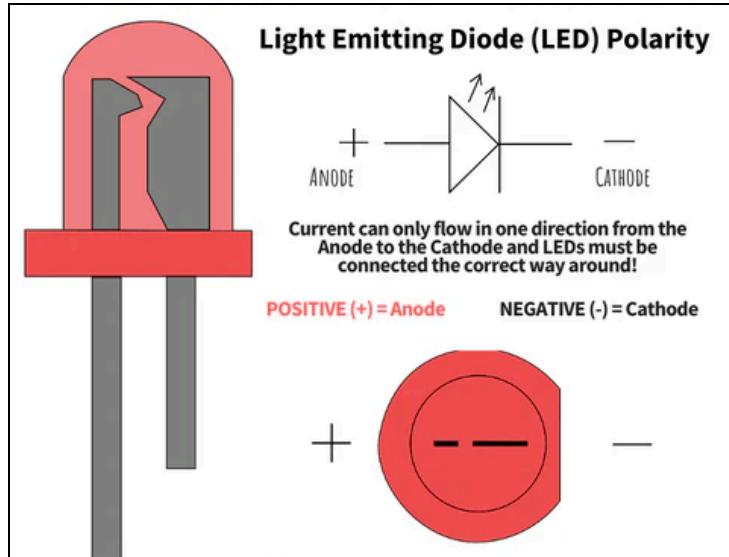


Fig 3.3.3: Diode Orientation ([link](#))

My diode has the opposite of leg to flat edge, I will ask a TA. I ended up checking the continuity, as diodes have one-way (effective) short circuits. It ended up being the edge that is flat.

## Mounting the RS-232

Setting the RS-232 was relatively easy, and I just broke off 9 pins from the long strands of pins I had. Make sure to put the long ends through the board, such that the black pieces end up on the top!

Future note: it may be easier to get another person/something to hold the pins in place for solder, it will prevent the tilting the occurred.

## Wire Standards

For this project I will follow the conventional wire colors specified from the lab instructions:

Signal Type	Color
Power	Red
Ground	Black
Multiplexed Address/Data	Grey
Buffered Data	Yellow

Latched Address	Blue/Dark Orange (as blue is not available)
Control Signals	Orange
Serial Port Signals	Green

## Wire Wrapping

Wire Wrapping demon [link](#)

Instructions:

1. Get a wire wrapping tool
  - a. Body
  - b. Stripper
  - c. Cap
2. Strip a wire with ~0.75" of metal exposed
3. Insert the wire into the small, semicircular hole (let it come out of the side of the wrapper)
4. Make sure the wire is long enough/has enough space to be wrapped around your other lead
  - a. It may be easy to strip the other side of the wire at this point
5. Place the pin within the large hole
6. Turn any direction
  - a. Be consistent in the direction you turn to take off wires easy
  - b. I chose clockwise

Taking wires off:

1. Insert the pin over the large hole
2. Turn in opposite direction you tightened the wire in with
  - a. This will be counter clockwise for me
3. Do not re-use unwrapped wires this way, as the ends are severely weakened

At this point for us, we have nothing to wire as we are using the board from 2005 that has wired GND and VCC for the controllers we have added so far.

## Verification

After plugging in the power, I got no voltage drop across the power supply. I had checked the continuity before between the middle and side pins, one of which had continuity, and thus I assumed both were ground. After plugging in the power supply, they no longer had continuity, so the circuit did not work. I swapped the wires out (and now have a big solder blob on the back of my board), and the LED still did not come on. Turns out I forgot to add the jumper for power. Now the LED turns on just fine when the board powers up, and all the 5V rails are 4.996 V to

ground with the multi meter. (I also had unsoldered discharge capacitors that were shorting ground and 5V, but I fixed it when I realized the 7805T was getting too hot)

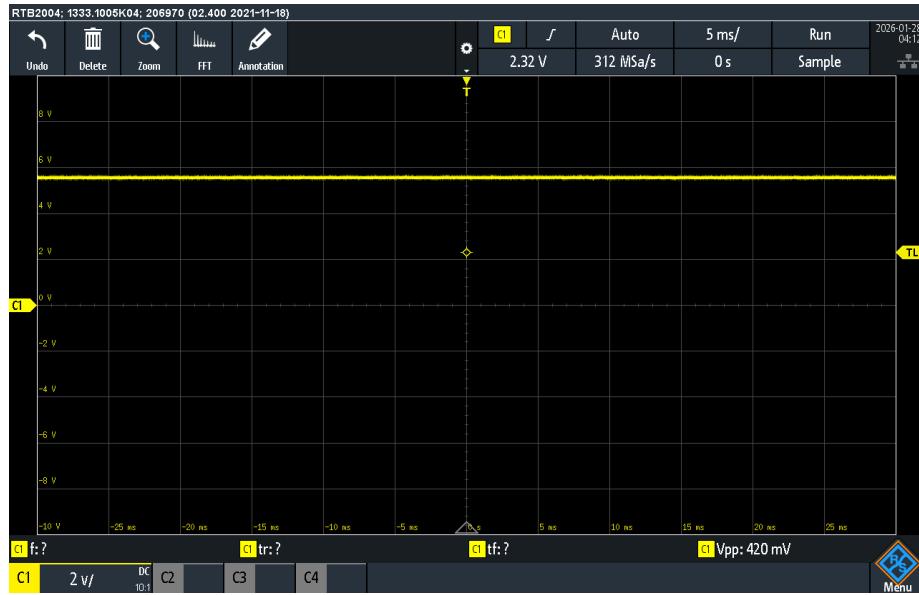


Fig 3.4.1: Stable 5V signal from O-scope

## Oscillator circuit

### Solder

- Oscillator
- 2x 27pF capacitor C5 & C6

Also add the decoupling caps for C20 and C21 (100nF)

## Pre-Programming

Pull up port 0 pins: using line resistor:

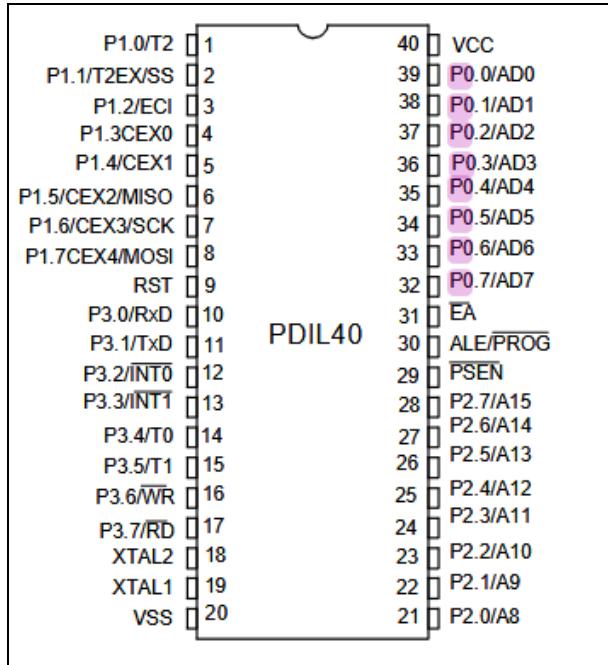


Fig 3.5.1: Port 0 pins (page 9 of datasheet)

Tie EA line high (part of the line of resistors we put in)

## Programming

Download the hex file from canvas and take 8051 over to station and use Phyton to load the file onto the chip (see “Programming the Atmel ATF16V8C SPLD with the Phyton ChipProg-48 Device Programmer” on canvas.

# Validation of Circuit

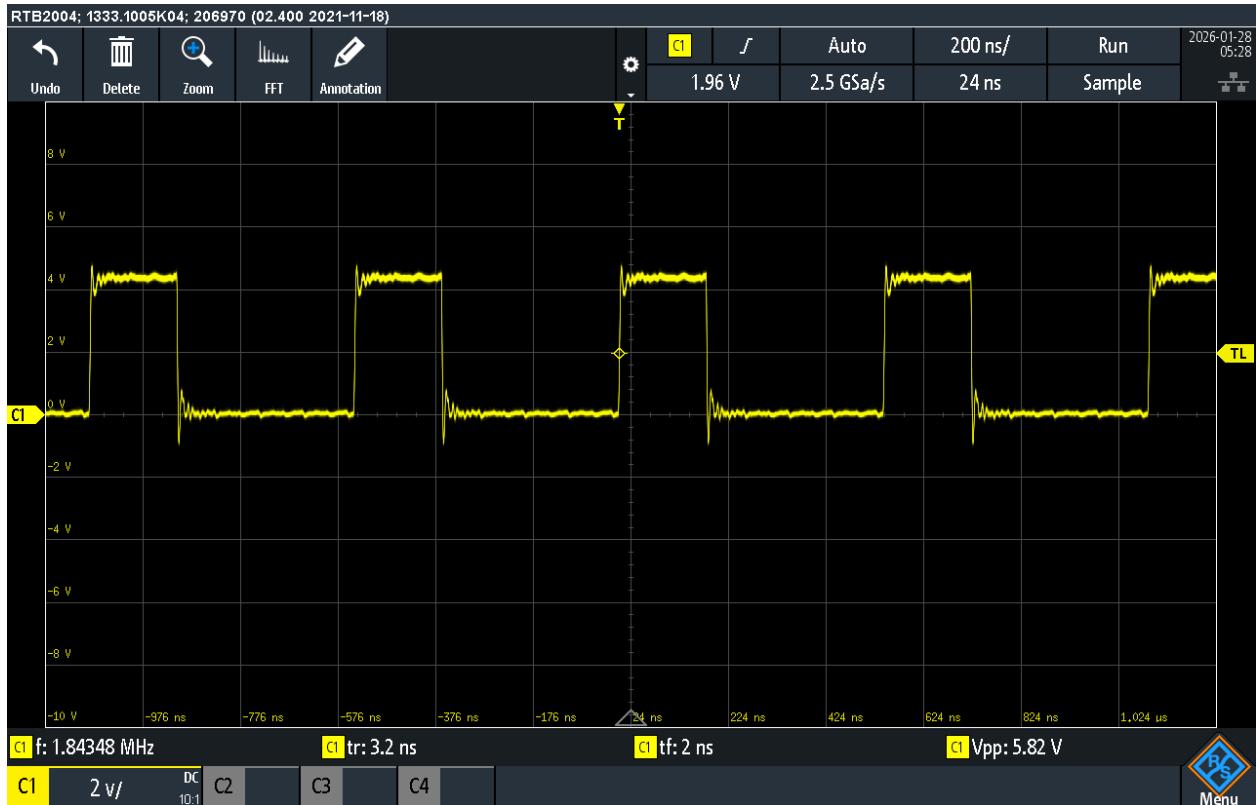


Fig: 3.6.1: Ale line output after flashing code

Notice the ringing that is occurring. This is due to the scope probe (and is not caused by compensation). I stole a screwdriver from capstone to check that I have returned. This ringing can also be seen on the compensation line.


Crystal oscillator: ~11.0592 MHz

Estimated ALE line frequency: ~1.8432 MHz

Measured ALE line frequency: 1.8435 MHz

This discrepancy is easily explained within nominal ranges for our environment


This circuit worked on every press of rest & off/on toggle, thus I did not compensate the capacitors

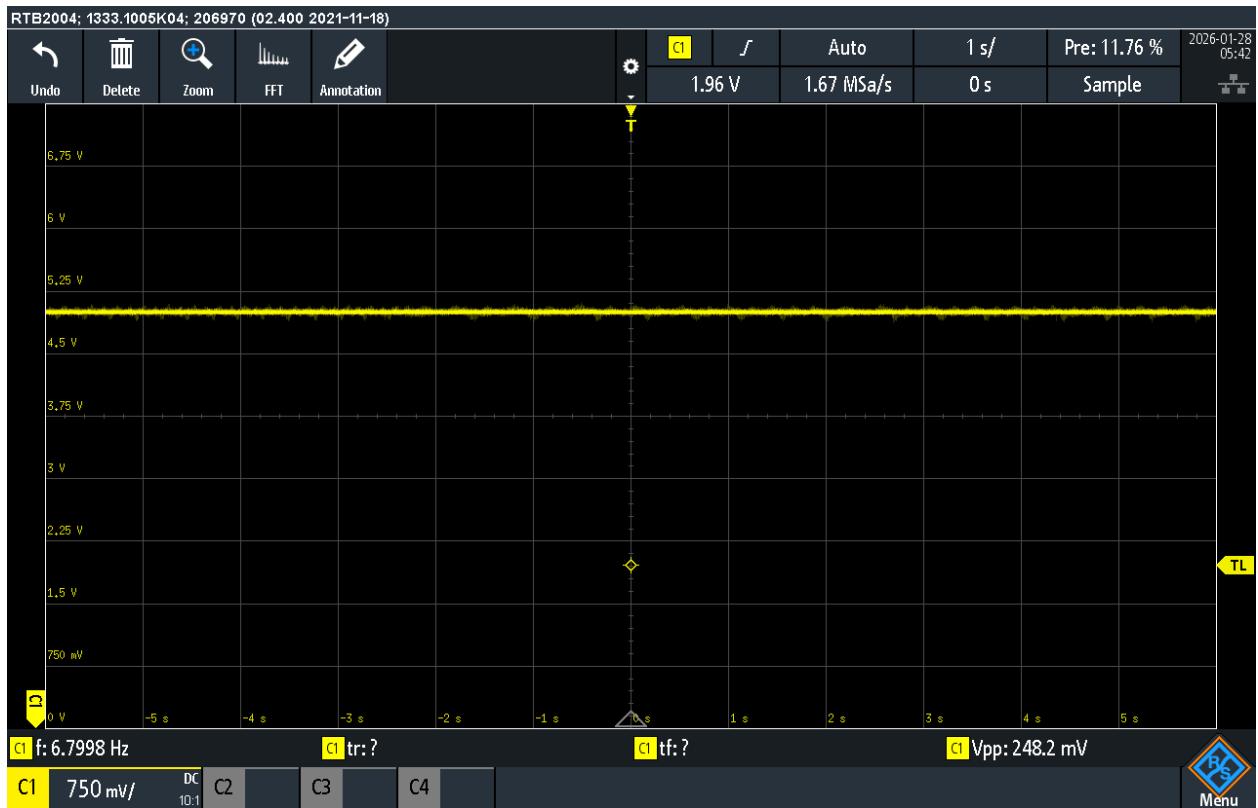

**Fig 3.6.2: Scope probe of VCC and GND over 1s**

We can see that the oscillation is much less than 800mV at 248.2 mV.

## Wiring the '373

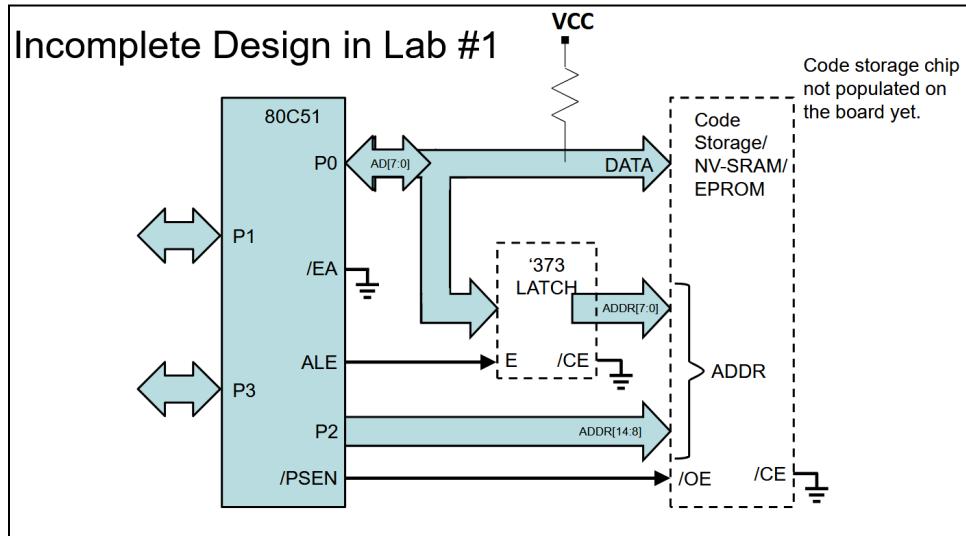

**Fig 3.7.1: Design of the '373 latch circuit (from lecture 3 slide 76)**

The D pins on the latch are the “input” (coming in from the microcontroller)  
The Q pins are the output pins

- AD0 => D0
- AD1 => D1
- Ect.

These have a wire color of Blue/Dark Orange (as blue is not available) as this data is a Latched Address

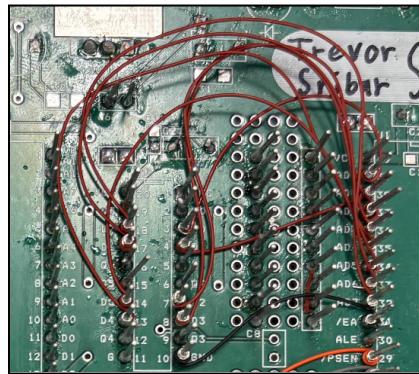


Fig 3.7.2: Wiring for '373 latch

## Wiring the SPLD (F16V8B)


From the earlier WinCurl code, modified to fit board layout:

```
/* ***** INPUT PINS *****/
```

```
PIN 2 = PSEN_n  
PIN 9 = RD_n  
PIN 4 = A15  
PIN 5 = A14  
PIN 6 = A13  
PIN 7 = A12
```

```
/* ***** OUTPUT PINS *****/
```


```
PIN 18 = READ_n  
PIN 19 = CSUPERIPH_n
```

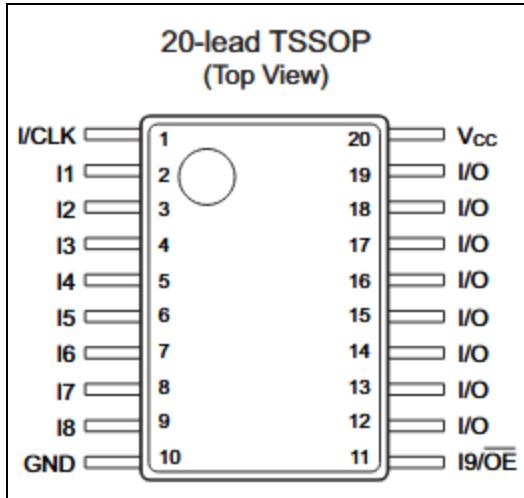

**Fig 3.8.1: Schematic for ATF16V8B**

Pins A12-A15 are address pins (Grey)

Pins PSEN\_n and RD\_n are control pins (Orange)

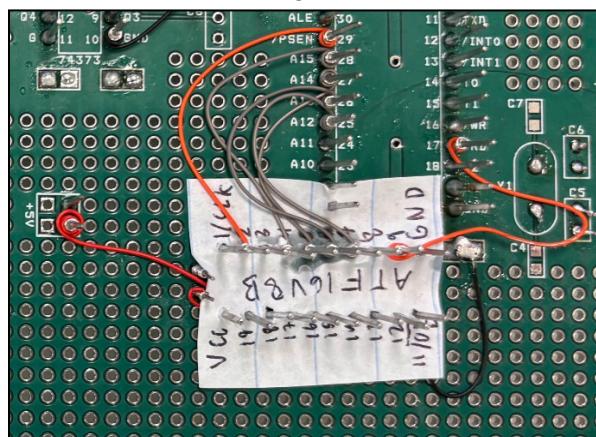

**Fig 3.8.2: Wire Wrapped SPLD**


## Loading Code to SPLD

Follow the steps outlined in the PhytonProgrammingATF16V8C found on canvas, this is the file name I gave it for my google drive (should be under Life -> School -> colleg -> 3nd 2st -> in bed system design)

## Verifying Output

I attached the latch, 8051, and the SPLD.

READ\_n output is as seen below, compared to /PSEN:

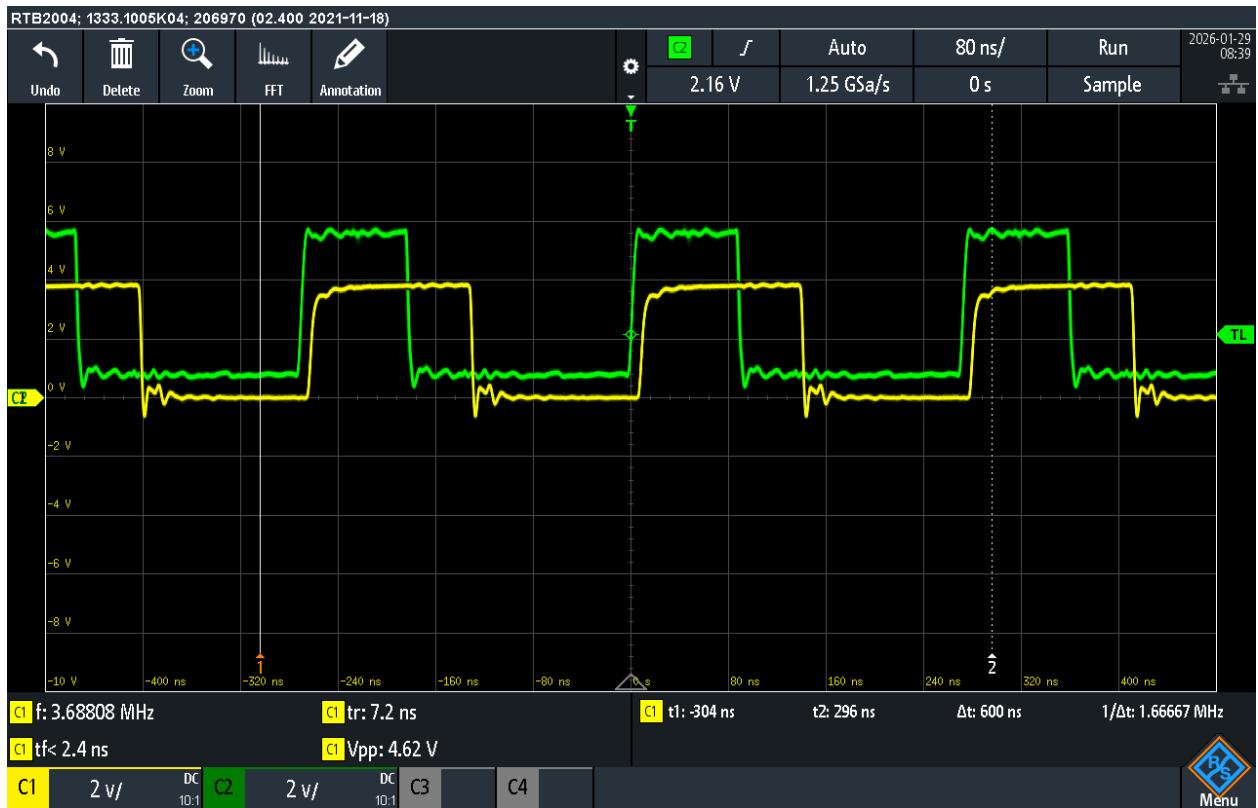

[test0124.hex](#)

Fig 3.8.2: Image of READ\_n with respect to /PSEN

CSPERIPH\_n output is as seen below:

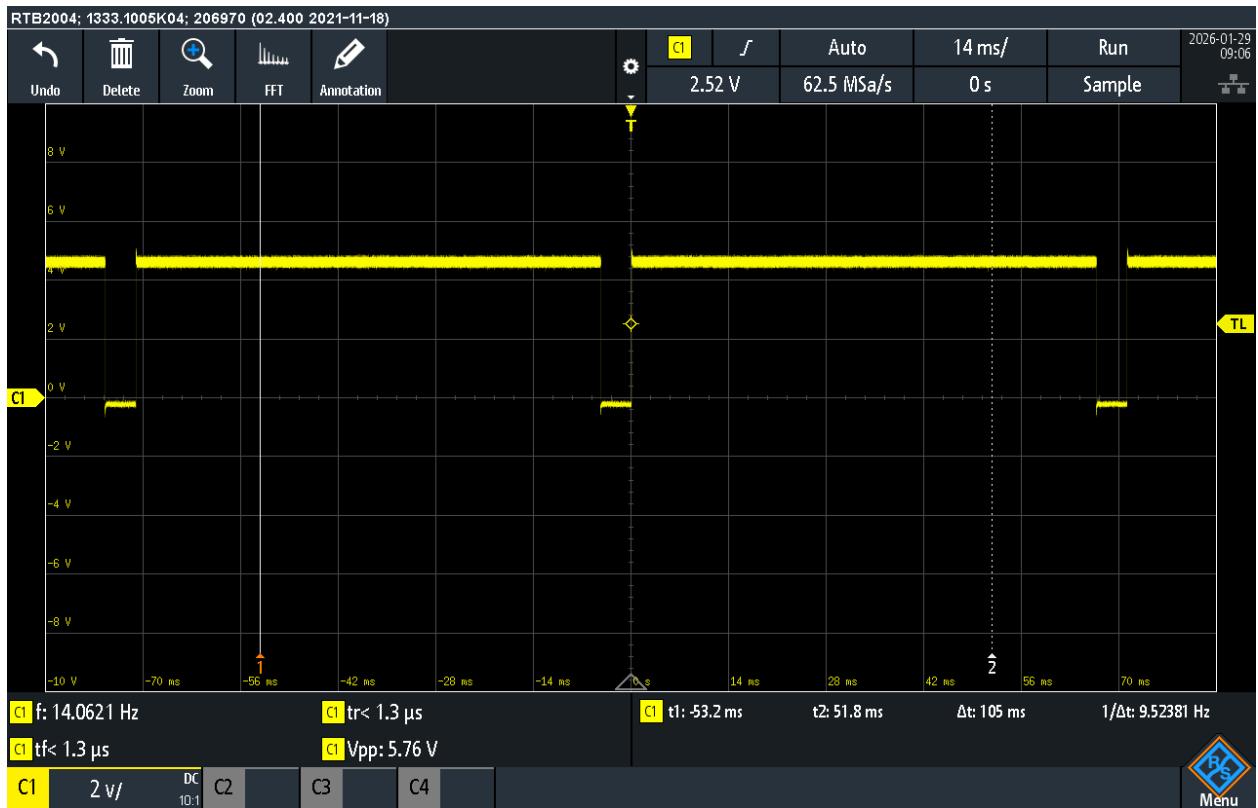


Fig: 3.8.3: Image of CSPERIPH (15/16 duty cycle)

## Oscilloscope:

FFT does a fast fourier transform: plots the magnitude of all present frequencies

## Future steps

For each element added

1. Check the closest VCC and GND
2. Check what you must connect to with the microcontroller
3. Build the expected final build into the schematic
4. Check the orientation of the chip (mirrored on the bottom of the board)
5. Check continuity after wiring/soldering

# EFM8BB1/ARM

## Basics of ARM

ARM is an instruction set architecture, so many processors can be arm processors, even if their functionality vastly differs. They are a part of RISC (Reduced Instruction Set Computer). They are light, low power, portable, making them good for embedded systems. It differed from the normal RISC processors by servicing interrupts, and has many other pieces that make them good for embedded systems.

## Our ARM Chip

Our ARM chip is an STM32F411, which can be programmed with CUBE32IDE, which has many functions similar to VS code such as control clicking to find function definitions. It is usually used to flash C code to the chip.


## Basic ARM Program

Logic: While the button is pressed, the LED will be on, otherwise it will turn off.  
This code can be seen in the final lab submission.

## Questions and Check in


**What voltage is present at the regulator input?**

7.709 V

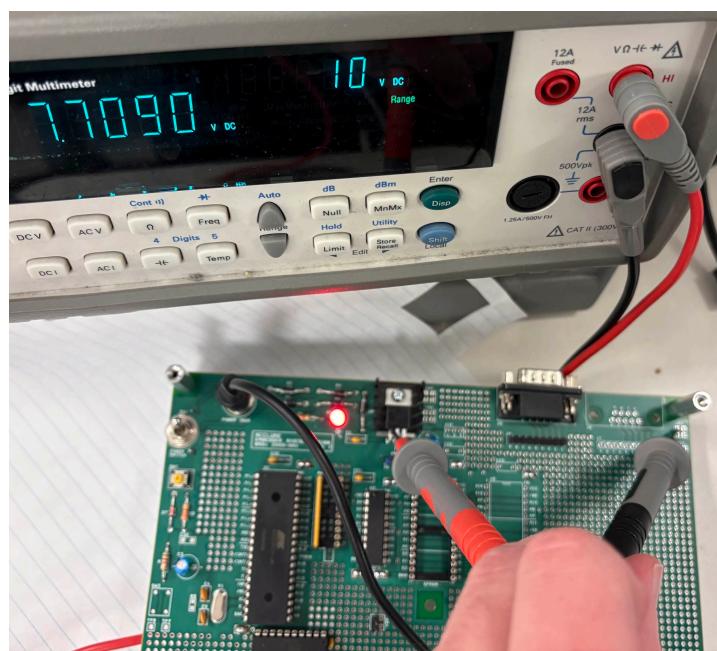

**What voltage is present at the regulator output?**

4.9976 V

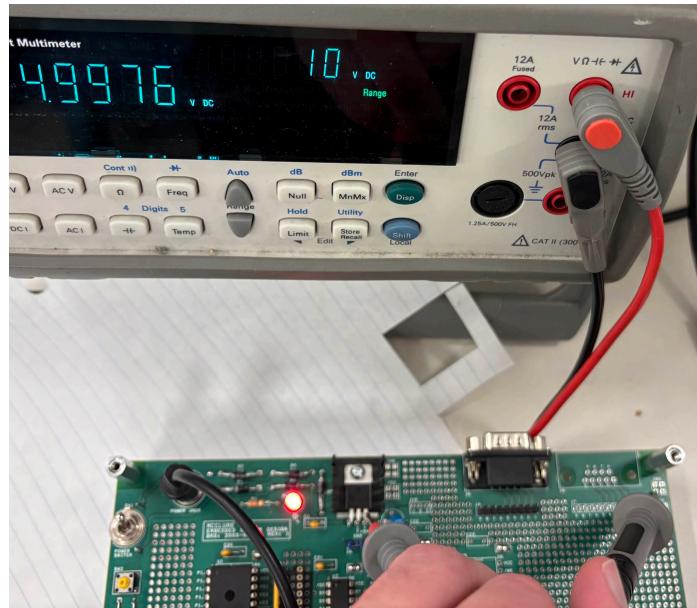

**What peak to peak noise is present across the processor VCC and GND?**

Measured value at processor package pins on top side of board: 480mV

Measured value at wire wrap socket pins on bottom side of board: 440mV



Left is top PIN (inserting probe into VCC location), Right is bottom side location of wire wrapping, that directly links into top pin.

**How long is the processor held in reset after the run-time reset pushbutton is released?**

**Use an oscilloscope and try to measure the time between the release of the pushbutton and the time when noise from ALE is observed on the RST signal.**


Measured value: ~37.5 ms



C2 is the reset pin, C1 is the ALE pin

**What frequency is present at the ALE pin?**

1.84348 MHz

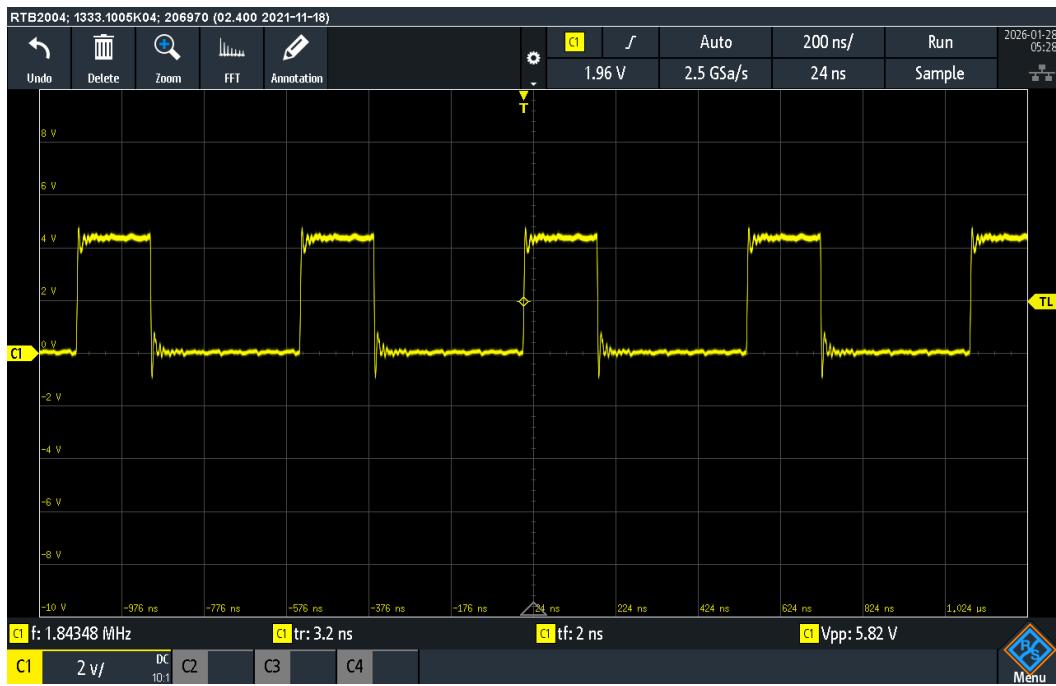

Probing of ALE pin

**How much power is dissipated in the regulator, assuming a load current of 160mA?**  
**Assume that the regulator is drawing the max quiescent current shown in the data sheet**  
**(use the correct data sheet for the regulator you have on your board). Neatly show all**  
**your work and be able to explain how current flows into and out of the regulator.**

Calculated value: 437.6785 mW

From Slide 51 of Lecture 3:

$$P_{REG} = ((V_{IN} - V_{OUT}) * I_{LOAD}) + (V_{IN} * I_G)$$


We have all but  $I_G$  from the earlier parts, and from the datasheet:

$\Delta I_Q$	Quiescent Current	$5 \text{ mA} \leq I_Q \leq 1\text{A}$	0.5	mA
--------------	-------------------	--	-----	----


$V_{in} = 7.709$	X
-10	10
$V_{out} = 4.9976$	X
-10	10
$I_{load} = 160 \cdot 10^{-3}$	X
= 0.16	
$I_g = 0.5 \cdot 10^{-3}$	X
= 0.0005	
$P_{REG} = ((V_{in} - V_{out}) \cdot I_{load}) + (V_{in} \cdot I_g)$	X
= 0.4376785	

Calculations for power dissipated in regulator

Which gives 437.6785 mW

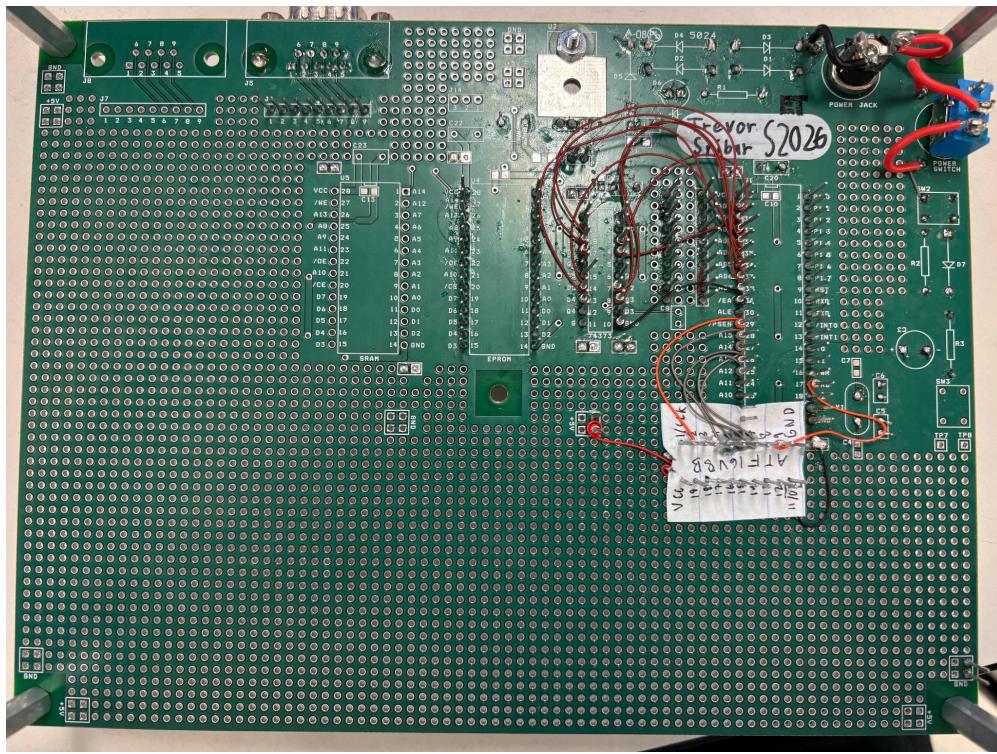

**Fig 4.1.1: Final board picture BACK**

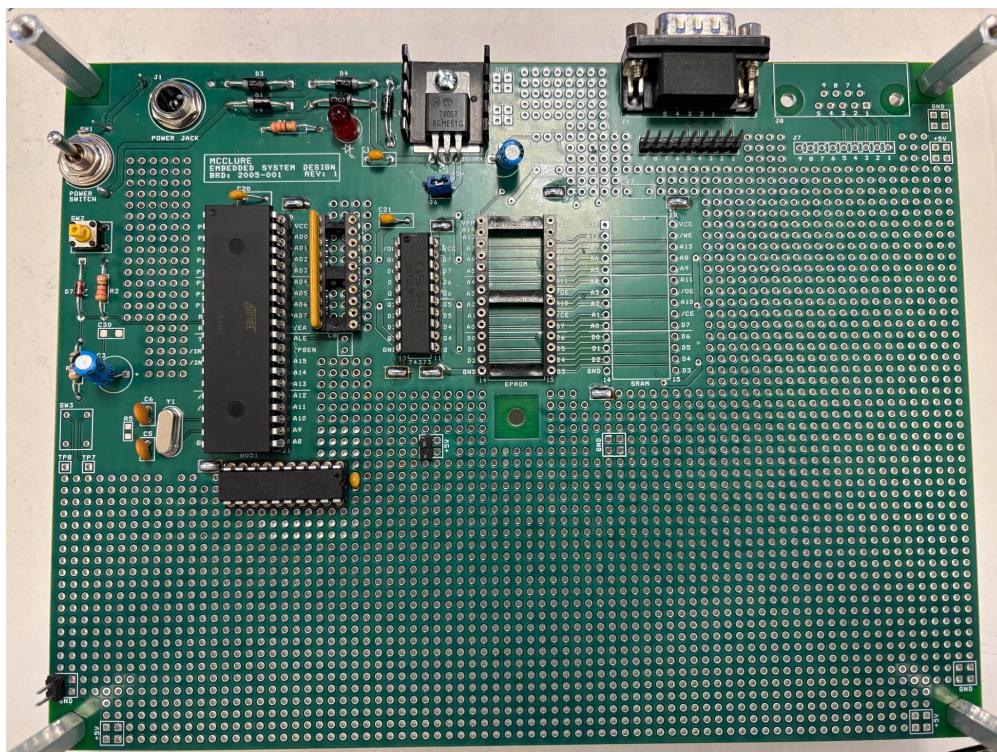

**Fig 4.1.2: Final Image of Board Front**